

CONTINUOUS INTERNAL EVALUATION - 2

Dept:EC	Sem / Div:3 A&B	Sub: Network Theory	S Code:18EC32
Date:1/12/20	Time: 2:30-4:00PM	Max Marks: 50	Elective: N

Note: Answer any 2 full questions, choosing one full question from each part.

QN	Questions	Marks	RBT	CO's
----	-----------	-------	-----	------

PART A

1	a Find the Z parameters and h parameters for the circuit shown in fig 1(a)	9	L3	CO4
---	--	---	----	-----

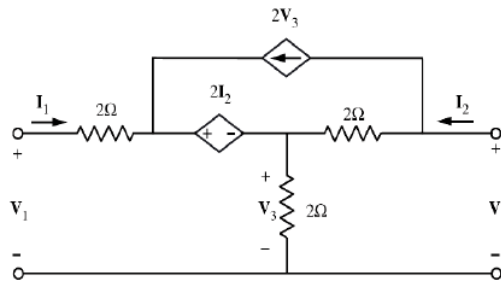


fig 1(a)

	b Derive the expression for bandwidth of a series resonant circuit.	8	L2	CO4
--	---	---	----	-----

	c Find the value of RL for maximum power transfer and value of maximum power that is transferred to the load in the circuit 1.c	8	L3	CO2
--	---	---	----	-----

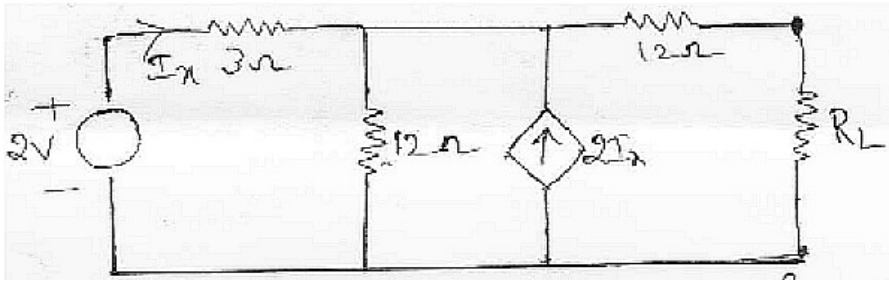


Fig 1.c

OR

2	a Find the y parameters and z parameters for the circuit in fig 2(a).	10	L3	CO4
---	---	----	----	-----

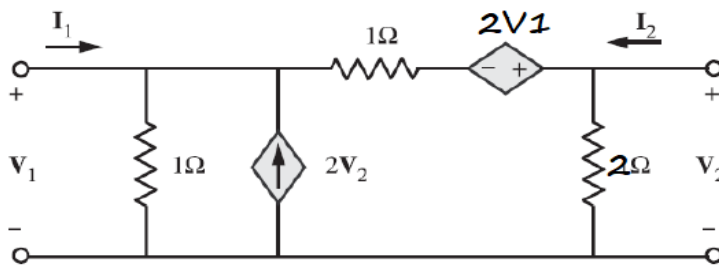


fig 2(a)

	b A series circuit with $R= 10\Omega$, $L=0.3H$ and $C= 100\mu F$ is connected across a 230V ac variable frequency supply. Find the i) resonant frequency, ii) half power frequencies, iii) bandwidth, iv) Quality factor, v) Current at	6	L2	CO4
--	---	---	----	-----

	resonance, vi) Current at half power frequencies and voltage across inductance at resonance			
c	Find the value of R_L to be connected across a-b for maximum power transfer	9	L2	CO2

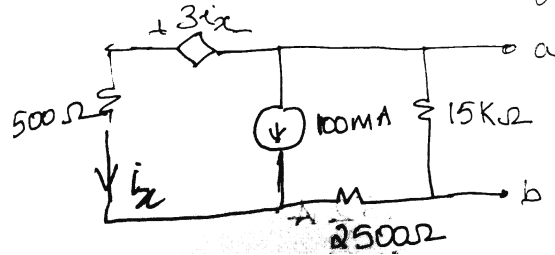


Fig 2.c

PART B

3 a	Determine the y parameters for the network in fig 3(a)	10	L3	CO4
-----	--	----	----	-----

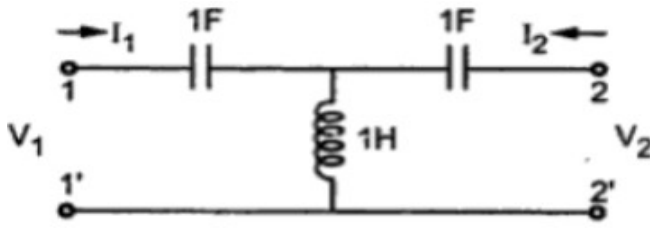


fig 3.a

b	For the circuit shown find the value of C for the circuit to resonate when the input supplied to the circuit is 125V at 50Hz.	5	L2	CO4
---	---	---	----	-----

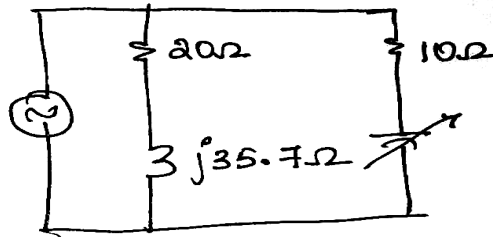


Fig 3.b

c	Find the value of R_L to be connected across a-b for maximum power transfer	10	L3	CO2
---	---	----	----	-----

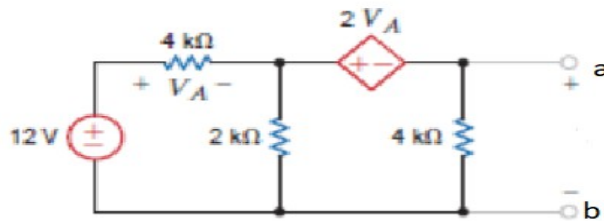


Fig 3.c

OR

4 a	Define ABCD parameters and express ABCD parameters in terms of Z and h parameters	10	L2	CO4
b	For the circuit shown in fig 4.b find ω_r , Q, BW, half power frequencies and output voltage V at ω_r .	10	L4	CO4

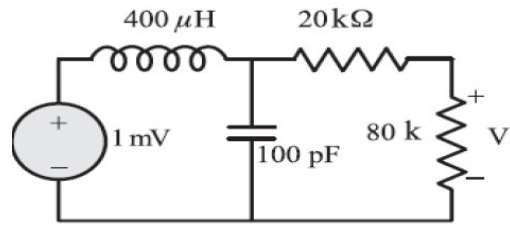


Fig 4. b

c Find the value of Z_L for which maximum power is transferred to the circuit.

5

L3

CO2

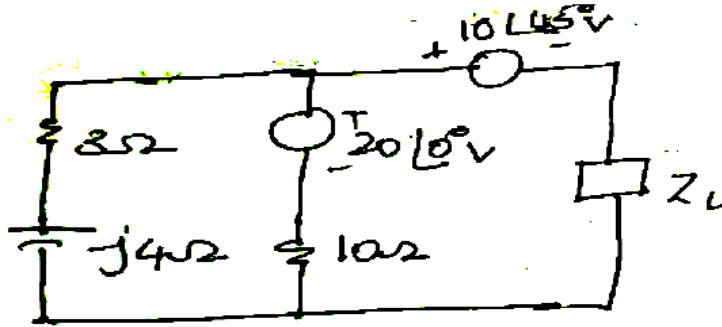


Fig 4.c

